

Capacitor Discharge

Jay Grinols

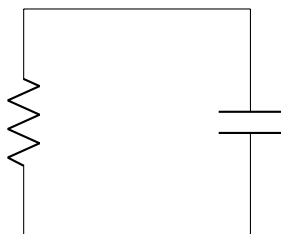


Figure 1: Setup of our circuit.

The capacitance is defined as $C = \frac{Q}{\Delta V_C}$. We know that $I \cdot R = \Delta V_R$ from Ohm's Law. By Kirchhoff's Loop Rule, we know that the sum of differences in potential in a closed loop must be equal to 0.

$$\Delta V_C - \Delta V_R = 0$$

Substituting for ΔV , we obtain that

$$\frac{Q}{C} - I \cdot R = 0$$

Recall that $I = -\frac{dQ}{dt}$, since the capacitor is losing charge. Solving for the

first order separable differential equation...

$$\begin{aligned}\frac{Q}{C} - I \cdot R &= 0 \\ \frac{Q}{C} + \frac{dQ}{dt} \cdot R &= 0 \\ \frac{dQ}{dt} \cdot R &= -\frac{Q}{C} \\ \int \frac{dQ}{Q} &= - \int \frac{dt}{R \cdot C} \\ \ln Q &= -\frac{1}{R \cdot C} \cdot t + C_1 \\ Q(t) &= C_2 \cdot e^{-\frac{t}{\tau}}\end{aligned}$$

We know that $Q(t) = C \cdot \Delta V_C(t)$, and that $Q(0) = C \cdot \Delta V_0$.

$$\begin{aligned}C \cdot \Delta V_0 &= C_2 \\ Q(t) &= C \cdot \Delta V_0 \cdot e^{-\frac{t}{\tau}} \\ C \cdot \Delta V_C(t) &= C \cdot \Delta V_0 \cdot e^{-\frac{t}{\tau}} \\ \Delta V_C(t) &= \Delta V_0 \cdot e^{-\frac{t}{\tau}} \\ \ln \Delta V_C(t) &= -\frac{1}{\tau} \cdot t + \ln \Delta V_0\end{aligned}$$